

LDO WITH HIGH PSRR

VL804 : ANALOG POWER IC DESIGN

MAY 10, 2024

1. Malobi Mukherjee - MS2023006
2. Vartika Barnwal - MT2023535
3. Akhil Ganesh Asati -MT2023502
4. Pratikkumar AshokKumar Solanki - MT2023527

CONTENTS

- **Specification Table**
- **Circuit Diagram**
- **Key Challenges Addressed**
- **Theoretical analysis or Design approach**
- **Simulation result-1 (DC-operating points – Schematic snapshot)**
- **Simulation result-2 (AC analysis/Loop gain, plots)**
- **Simulation result-3 (PSRR plots)**
- **Simulation result-4(Load transient plots)**
- **Simulation result-6 (Line and Load regulation plots)**
- **Simulation Results Table**
- **Backup Paper and Project Slides**

□ Key Challenges Addressed

- Increase PSRR Value by using suitable value of C_c Miller Capacitance
- Enhance the value of PSRR at High Frequency (MHz) range
- Implemented paper A 65-nm CMOS Low Dropout Regulator Featuring >60-dB PSRR Over 10-MHz Frequency Range and 100-mA Load Current Range


Reference Paper Specification Table

		Units	Paper 1	Paper 2	Paper 3	Paper 4	Paper 5	Paper 6
Techniques								
Technology		nm	65	180	130	180	90	180
Power Transistor			NMOS					PMOS
Maximium ILoad		mA	100		25	200	140	
Nominal Vin		V	1.2	8-45	>1.15	1.8-2.5	>1.15	
Vout		V	1	5	1	1.6-2.5	1	
Minimum Dropout		V	80		>0.15	0.2	>0.15	0.178
Cout		uF	4.7			1		
Load Regulation		uV/mA	10					
Quiescent Current		uA	40		50	0.6-160	33-145	5.6-35.6
Overshoot		mV	2					28.7
Undershoot		mV	4					36.36
PSRR Heavy Load	ILoad	mA	100	50	25	200		250
	100KHz	dB	89		60		53	80
	1MHz	dB	70	70	67	40.5	62	70
	10MHz	dB	62	57	56		56	60
PSRR Light Load	ILoad=	uA	100					
	100kHz	dB	81					
	1MHz	dB	75					
	10MHz	dB	91					
Area		mm^2	0.048		0.0049	0.037	0.015	0.12
Iout(max)		mA	50					
Line Regulation		mV/V		0.0397	26	4.86		
Load Regulation		mV/mA		0.00018	0.048	0.055	0.043	0.112


Used Specification Table

Parameters	Units	Values
Supply Voltage	V	2.1
Output Voltage	V	1.8
Dropout Voltage	V	0.2
Dropout Voltage	V	0.2
C_Load	nF	200
Quiescent Current	uA	25
I_Load(maximum)	mA	50
I_Load(minimum)	mA	10
PSRR(@ High Frequency)	dB	40.9
PSRR(@ Low Frequency)	dB	70.8

□ Circuit Diagram(Schematic)

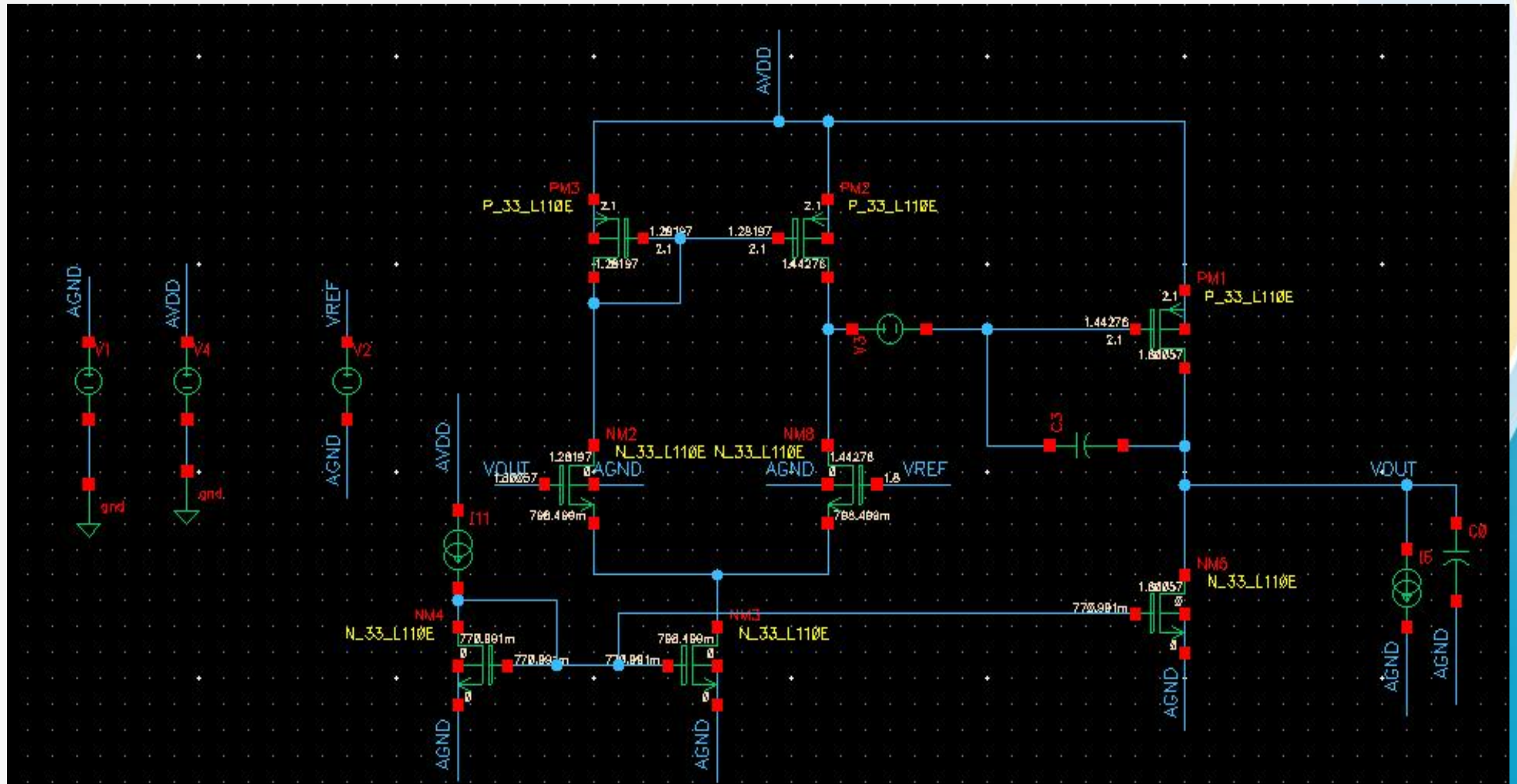

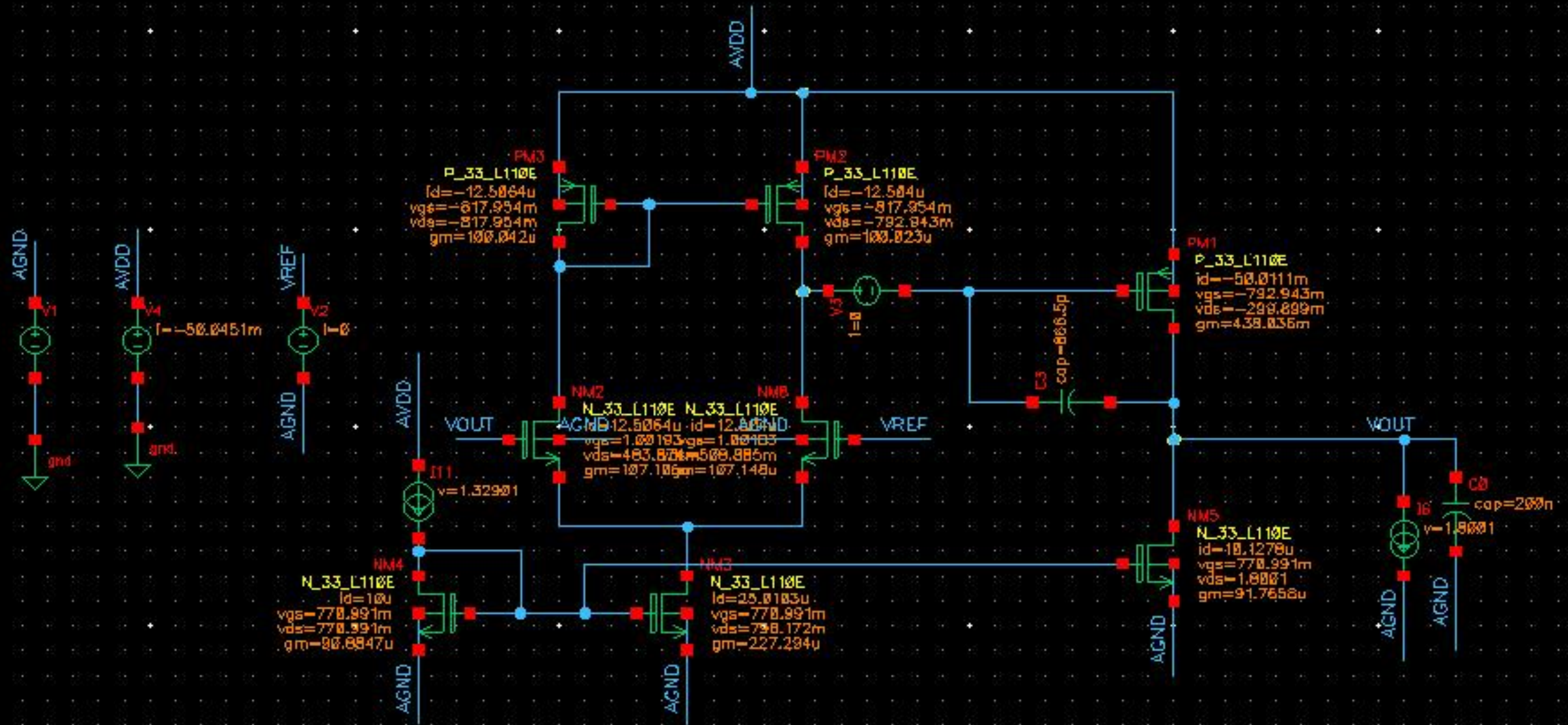Simulation Result-1 (DC Operating Points for Compensated 50mA)



❑ Theoretical Analysis or Design Approach

❑ DC Operating Point Values of All Transistor at $I_{Load}=50mA$

Mosfet	NM5	NM2	NM4	NM3	NM1	NM0	PM3	PM2	PM0	PM1	PM7
Vov(V)	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2	0.2
Vth(V)	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6	0.6
Vgs(V)	7.71E-01	7.68E-01	7.71E-01	7.68E-01	7.74E-01	7.74E-01	7.89E-01	7.89E-01	7.89E-01	7.89E-01	7.76E-01
Vds(V)	7.71E-01	7.68E-01	2.26E-01	7.68E-01	1.85E-01	1.85E-01	4.32E-01	7.89E-01	7.89E-01	7.76E-01	2.00E-01
rout(ohm)	6.49E+06	1.32E+06	3.37E+04	1.32E+06	2.53E+04	2.53E+04	7.88E+05	2.65E+06	2.65E+06	7.96E+05	2.03E+05
Vgt(V)	1.86E-01	1.82E-01	1.86E-01	1.82E-01	1.88E-01	1.88E-01	1.96E-01	1.96E-01	1.96E-01	1.96E-01	1.83E-01
Ids(A)	1.00E-05	4.85E-05	9.74E-05	4.85E-05	4.87E-05	4.87E-05	4.85E-05	4.87E-05	4.87E-05	4.87E-05	8.34E-06
gm(S)	9.08E-05	4.46E-04	8.69E-04	4.46E-04	4.17E-04	4.17E-04	4.36E-04	4.37E-04	4.37E-04	4.35E-04	7.63E-05
Cgs(F)	6.86E-13	3.42E-12	6.83E-12	3.42E-15	3.36E-12	3.36E-12	1.16E-11	1.16E-11	1.16E-11	1.16E-11	2.29E-12
Cgd(F)	8.78E-15	4.39E-14	4.93E-13	4.39E-14	4.61E-13	4.61E-13	2.39E-13	2.03E-13	2.03E-13	2.04E-13	1.34E-13
region	2	2	2	2	2	2	2	2	2	2	2
Vds (sat) (V)	1.64E-01	1.61E-01	1.64E-01	1.61E-01	1.65E-01	1.65E-01	1.66E-01	1.66E-01	1.66E-01	1.66E-01	1.57E-01
self gain	589.23	592.976	29.273	592.97	10.57	10.57	345.961	1.15E+03	1.15E+03	1.14E+03	15.5135

□ Light Load ILoad=10mA with Compensation


Theoretical Calculation

Light Load with Compensation						
Pole 1-(Inside)(Hz)	1/((((1+Apass)*Cc)+Cgd(PM2)+Cgd(NM8)+Cgg(PM1))*(rout(NM8) rout(PM2)))				1.088075235	0.173260388
	3.174E-07	2895570.311	rout(NM8)	4.54E+06	rout(PM2)	7.99E+06
Pole 2- near Cload(Hz)	gm(PM1)/Cload					
	gm(PM1)	1.56E-01	Cload	2.00E-07	778460	
					123958.5987	
Mirror Pole (Hz)	1/((Cgd(NM2)+Cgs(PM3)+Cgg(PM2))*(rout(NM2) rout(PM3) 1/gm(PM3)))				18905852.26	3010486.029
	5.31713E-12	9947.782887	rout(NM2)	2.80E+06	rout(PM3)	1.07E+07
Passfet Zero (Hz)	gm(PM1)/Cgd(PM1)		653152661.8	104005200.9		
	gm(PM1)	1.56E-01		Cgd(PM1)	2.38E-10	
Zero at input (Hz)	gm(NM2)/Cgd(NM2)		8831481420	1406286850		
	gm(NM2)	1.07E-04	Cgd(NM2)	1.21E-14		
Gain-Opamp (dB)	gm(NM2)*(rout(NM8) rout(PM2)		rout(NM8)	4.54E+06	rout(PM2)	7.99E+06
	gm(NM2)	1.07E-04	2895570.311	310.2314031		
Gain-passfet (dB)	gm(PM1)*(rout(PM1) rout(NM5)		rout(PM1)	2.26E+03	rout(NM5)	8.90E+06
	gm(PM1)	1.56E-01	2254.428665	350.9965077		
Total Gain				108890.1391		112689.6352
				100.73 dB		
w(ugf) (Hz)	18866.34772					


❑ Heavy Load ILoad=50mA with Compensation Theoretical Calculation & Cc Parameterization

Heavy Load with Compensation									
Pole 1-(Inside)(Hz)	$1/(((1+A_{pass}) \cdot C_c) + C_{gd}(PM2) + C_{gd}(NM8) + C_{gg}(PM1)) \cdot (r_{out}(NM8) \parallel r_{out}(PM2)))$					4.982269383	0.793354997	Cload	2.24E-07
	8.39864E-08	2389813.85	$r_{out}(NM8)$	3.11E+06	$r_{out}(PM2)$		1.03E+07	gmpass	4.38E-01
Pole 2- near Cload(Hz)	$g_m(PM1)/C_{load}$							gm(NM2)	1.07E-04
	$g_m(PM1)$	Cload						Cgd	2.38E-10
	4.38E-01	2.00E-07	2190180	348754.7771					
Mirror Pole (Hz)	$1/((C_{gd}(NM2) + C_{gs}(PM3) + C_{gg}(PM2)) \cdot (r_{out}(NM2) \parallel r_{out}(PM3) \parallel 1/g_m(PM3)))$					41883356.44	6669324.274		
	2.40012E-12	9947.77027	$r_{out}(NM2)$	2.80E+06	$r_{out}(PM3)$		1.07E+07		
			$g_m(PM3)$	1.00E-04		9992.605472		gmpass/CL	1955517.857
Passfet Zero (Hz)	$g_m(PM1)/C_{gd}(PM1)$		$g_m(PM1)$	Cgd(PM1)				(gmpass/CL)/2.2	888871.7532
			4.38E-01	3.33E-10		1315648625	209498188.6		
Zero at input (Hz)	$g_m(NM2)/C_{gd}(NM2)$		$g_m(NM2)$	Cgd(NM2)				((gmpass/CL)/2.2)/gm(NM2)	8299068701
			1.07E-04	1.21E-14		8837775394	1407289075	$1/(((gmpass/CL)/2.2)/gm(NM2))$	1.20495E-10
Gain-Opamp (dB)	$g_m(NM2) \cdot (r_{out}(NM8) \parallel r_{out}(PM2))$		$g_m(NM2)$	ROUT				Cc	-1.1787E-10
			1.07E-04	2389813.85		255.9610124			
Gain-passfet (dB)	$g_m(PM1) \cdot (r_{out}(PM1) \parallel r_{out}(NM5))$		$g_m(PM1)$	$r_{out}(PM1)$	$r_{out}(NM5)$				64.0219 pF
			4.38E-01	180.817	8.89E+06				
				180.8133224	79.20274448				
Total Gain	20272.81466	86.138 dB						Cc from parameterization	866.5p
Wugb(Hz)	16083.53882								

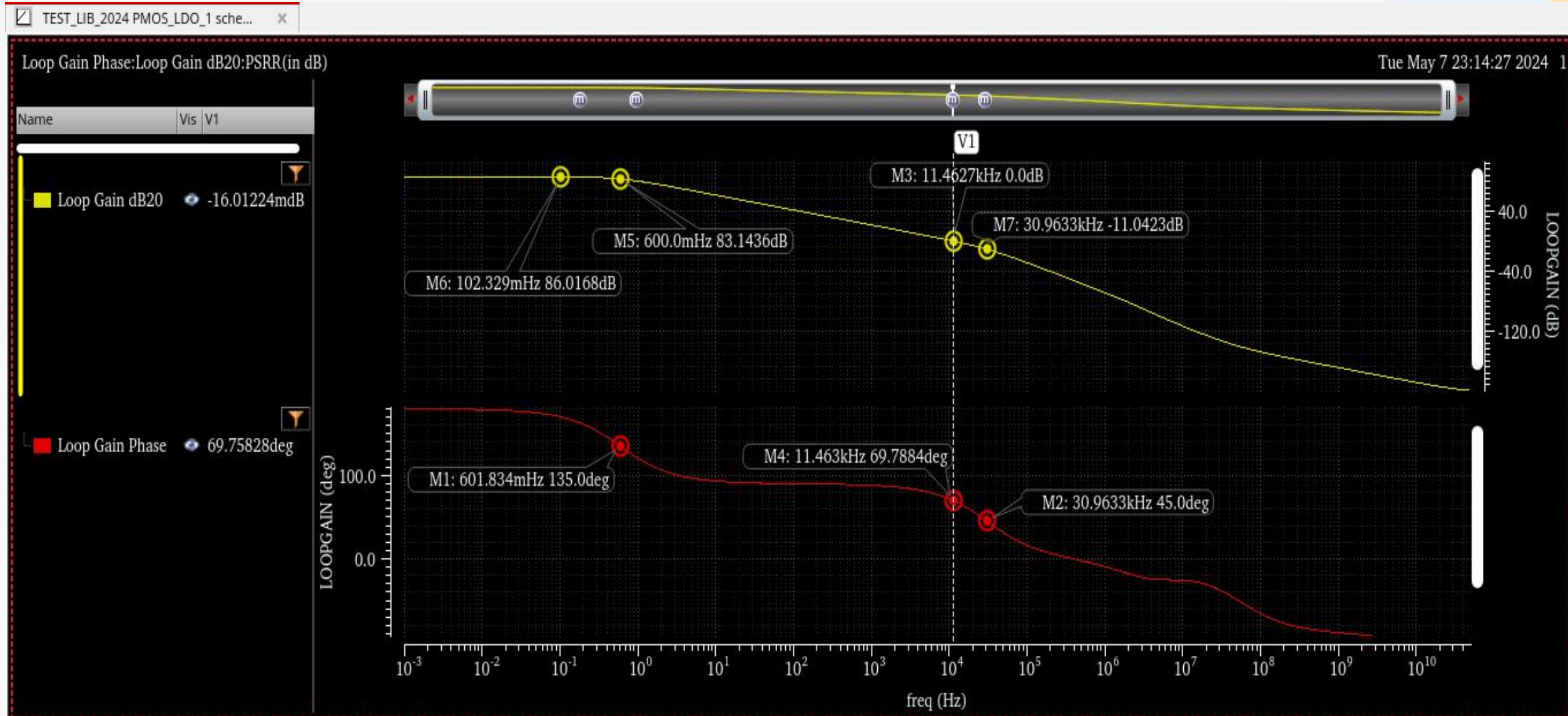Simulation Result-2 (Gain & Phase Plots For Compensated ILoad=50mA)



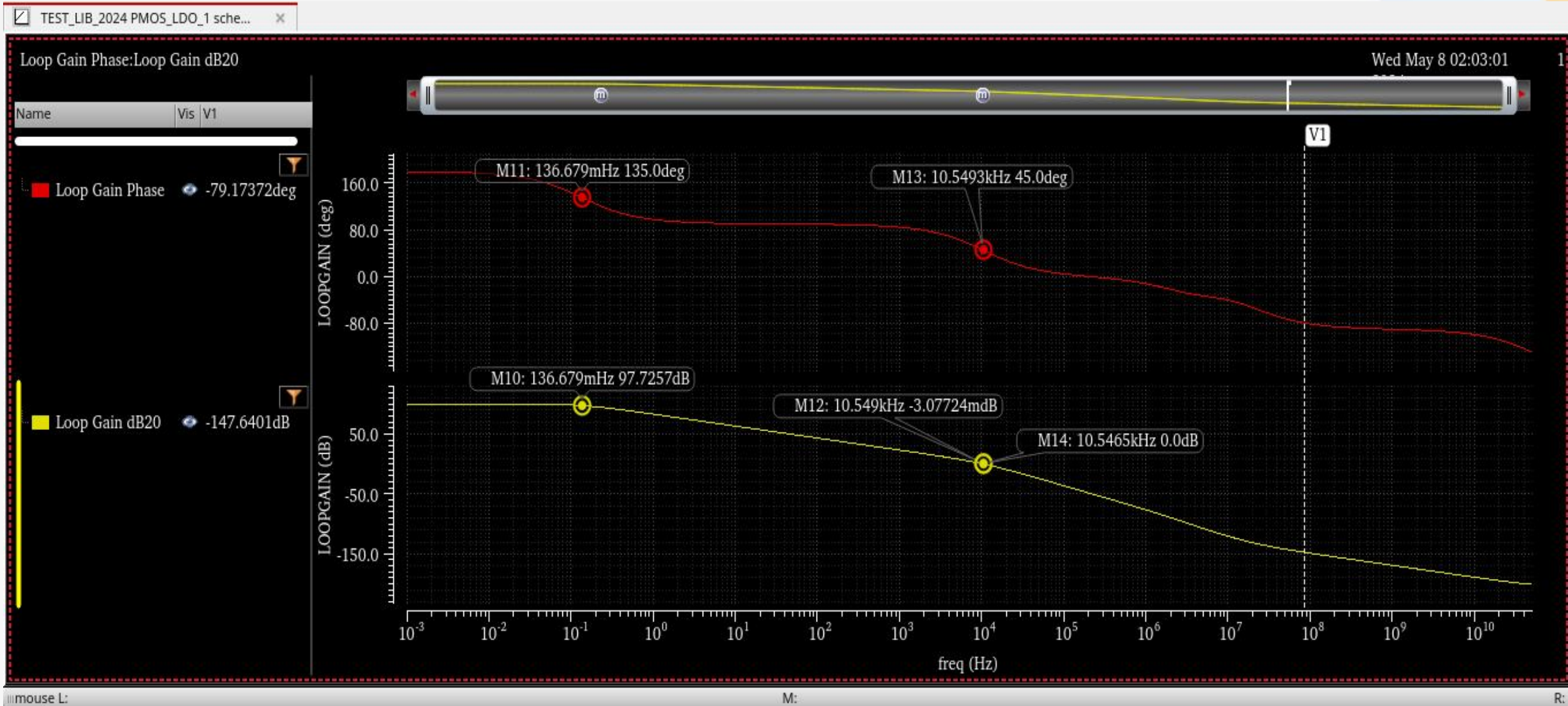
Simulation Result-2 (Gain & Phase Plots For Compensated ILoad=10mA)



Simulation Result-3 PSRR at ILoad=10mA




Simulation Result-3 PSRR at ILoad=50mA

 

Simulation Result-4 Load Transient(I_{Load}=50mA to 10 mA)

OVERSHOOT

Delta(VOUT) (V)	0.271
Delta(ILoad) (A)	0.04
Rout(DVOUT/DILoad) (ohm)	6.775

 


Simulation Result-4 Load Transient(I_{Load}=10mA to 50 mA)

UNDERSHOOT

Delta(V_{OUT}) (V) 1.414

Delta(I_{Load}) (A) 0.04

R_{out}(D_{VOUT}/D_ILoad) (ohm) 35.35

 


❑ Simulation Results Table


<u>SIMULATION RESULTS</u>		
Technology	110nm	
Input Voltage (Vin)	2.1V	
Load Current Max(ILoad_max)	50mA	
Load Current Min(ILoad_min)	10mA	
Output Voltage(VOUT)	1.8V	
Load Capacitance(Cout)	200nF	
Compesation Scheme	Miller(Internal) Compensation Cc	
PSRR @ 1Hz	70.80dB	
PSRR @ 1MHz	29.77dB	
PSRR @10MHz	41dB	
Load Overshoot Rout(ILoad=10mA to 50mA)	6.775 ohm	
Load Undershoot Rout(ILoad=50mA to 10mA)	35.35ohm	

Backup Slides

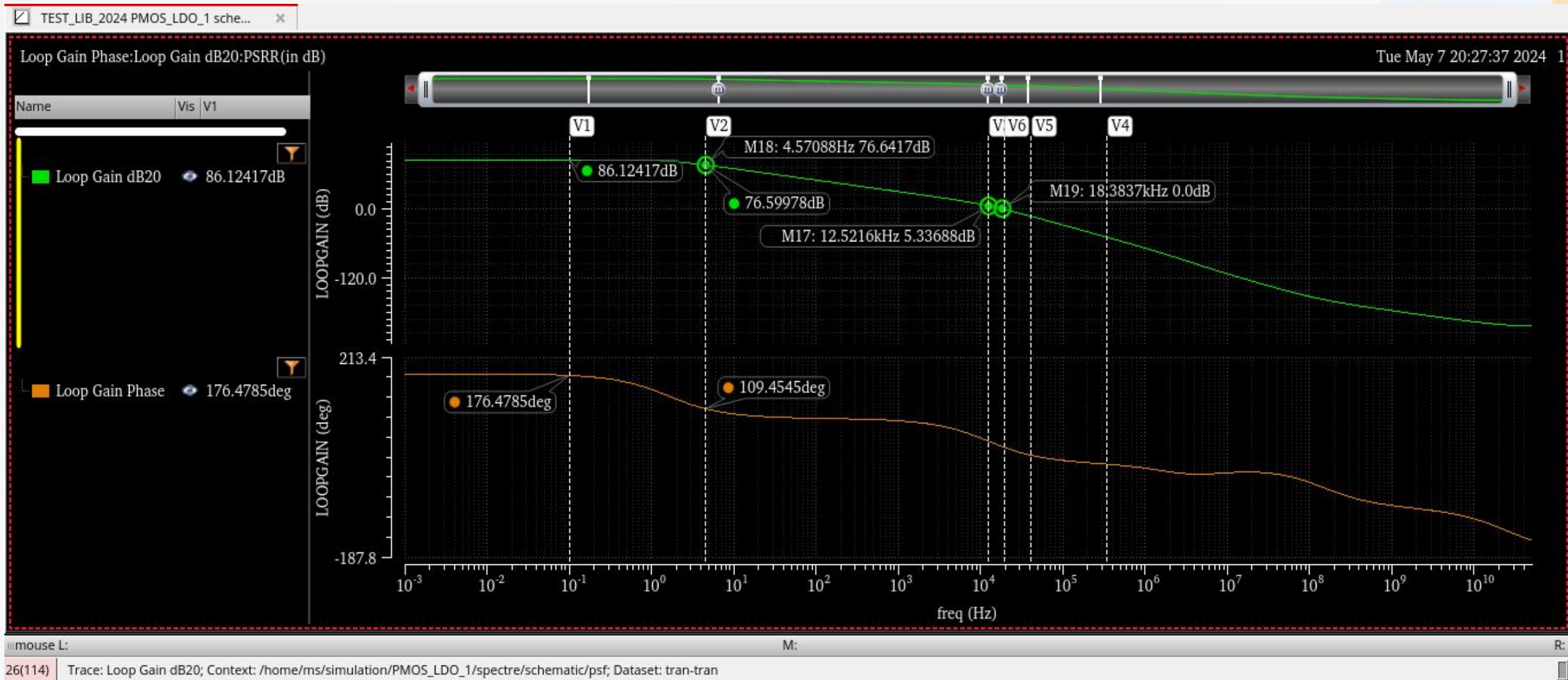❑ Simulation Result-2 (Gain & Phase Plots For Uncompensated ILoad=50mA)



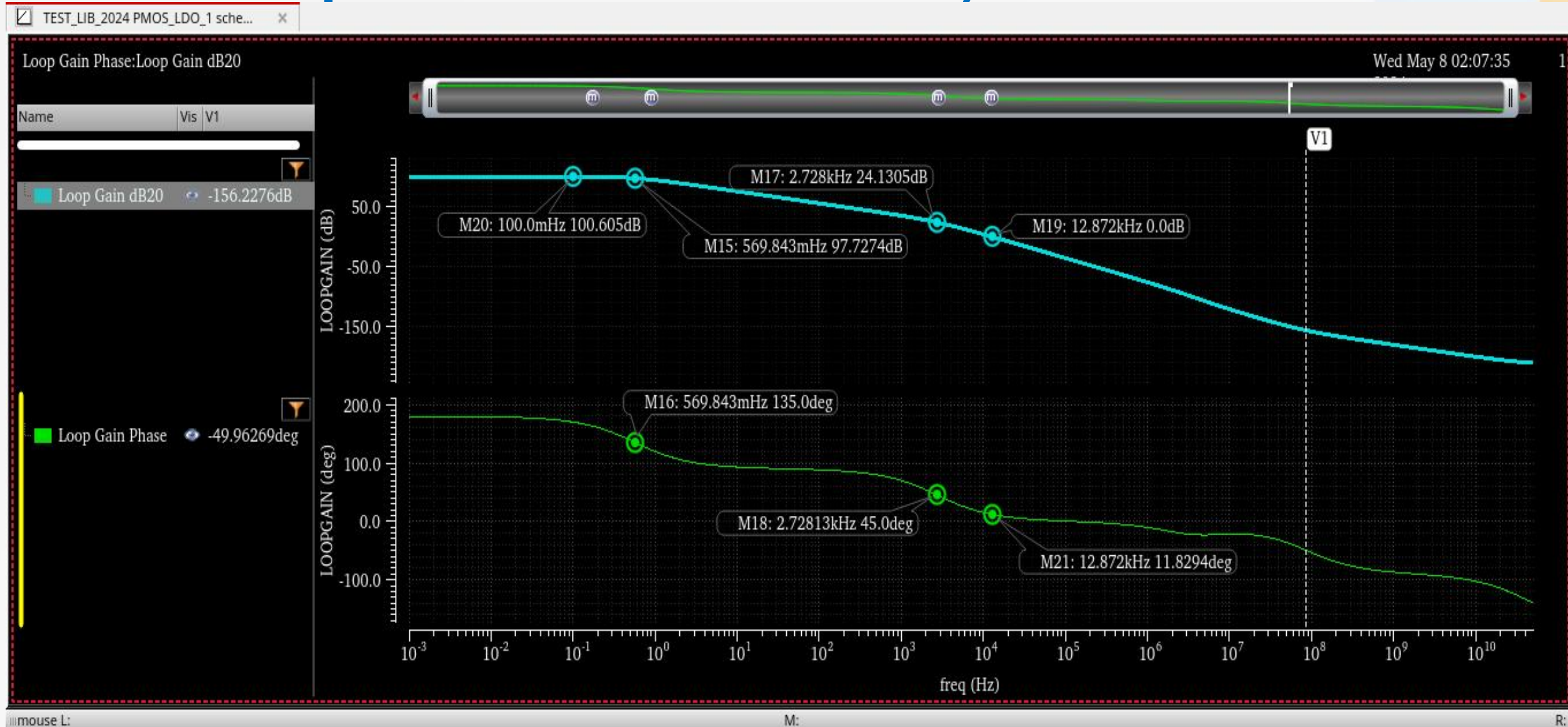Simulation Result-2 (Gain & Phase Plots For Uncompensated ILoad=10mA)



Reference Paper 1: A 65-nm CMOS Low Dropout Regulator Featuring >60-dB PSRR Over 10-MHz Frequency Range and 100-mA Load Current Range

- This paper presents an NMOS Passfet LDO, realized in 65-nm CMOS, featuring >60-dB PSRR over a 10-MHz frequency range and a 100-mA large load current range.
- The high PSRR is achieved by an adaptive feed forward ripple cancellation (FFRC) technique embodying an adaptive load current tracking scheme.
- By means of embodying an NMOS-based power stage, the LDO also achieves very low dropout voltage of 80 mV and features very small overshoot and undershoot of 2 and 4 mV respectively.

DC OPERATING POINT

Applications Places Virtuoso (R) Visualization & Analysis XL Sun 22:14

Virtuoso® Analog Design Environment L Editing: DCMOS_virtuoso_demo HIGHPSRR_LDO schematic

Launch File Edit View Create Check Options Window PVS UMC Utils Help

Navigator

- Schematic
- HIGHPSRR_LDO

OBJECTS

- All
- Instances 72
- Nets 42
- Pins 5
- Nets and Pins

GROUPS

- Cells
- Types

Property Editor

Schematic Attributes

- Library DCMOS_vir...
- Cell HIGHPSRR...
- View schematic
- Mode editable
- Last Saved Sun May 5...
- Locked By vlsiuser22...
- Units inch

mouse L: schSingleSelectPt()

M: geScroll(nil "w" nil)

R: schHiMousePopUp()

1(3) >

Cmd: Set: 0 Status: Ready T=27 C Simulator: spectre aps


vlsiuser22@visicadcli... [Virtuoso® 6.1.8-64b... Virtuoso® Analog De... ADE L (1) - DCMOS_... IEEE Xplore Full-Text ... [/home/vlsiuser22/... Parametric Analysis - ... Virtuoso (R) Visualiza... Pictures




Schematic HIGHPSRR LDO

- All
- Instances
- Nets
- Pins
- Nets and Pins

Cells
Types

 

Schemati Attributes

Library	DCMOS_vir...
Cell	HIGHPSRR...
View	schematic
Mode	 editable
Last Saved	Sun May 5...
Locked By	visiuser22...
Units	inch

R: schHiMousePopUp()

Cmd: Sel: 0	Status: Ready	T=27 C	Simulator: spectre aps
-------------	---------------	--------	------------------------


□ Theory Calculations

MOSFET	I(A)	W(m)	L(m)
nmos	1.00E-05	30.98u	8u
pmos	1.00E-05	115.971u	8u
nmos	1.40E-05	43.38u	8u
pmos	1.40E-05	162.36u	8u
nmos	8.00E-06	24.791u	8u
pmos	8.00E-06	92.77u	8u


	Rout	Cout	Rout*Cout	1/(Rout*Cout)
Pole (1 st)	4740395.2388	8.352735E-13	3.959527E-06	252555.44328 Hz
Pole (2 nd)	2297537.6922	4.162239E-12	9.562901E-06	104570.77841 Hz
Pole (3 rd)	8807104.4042	7.411472E-09	0.0652736095	15.320127199 Hz
Pole (4 th)	327.111	4.505755E-06	0.001473882	678.48035586 Hz
	GM	Cgs	gm/Cgs	
Zero(1st)	3.08E-01	5.76E-09	53499443.981	Hz
		Cgd		
Zero(2nd)	9.10E-05	5.50E-15	16545564611	Hz

DC gain of 1st stage	$gm(N1b) \cdot (rout(P1b+P2b) (N3b+N2b))$	rout(p1b)	rout(p2b)	rout(N3b)	rout(N2b)	gm(N1b)	Rout1	Rout2	Rout	Gain(v/v)
		3.88E+06	1.34E+07	6.53E+06	5.24E+06	9.10E-05	17275000	6533140	4740395.2388192	431.44707266
DC gain of 2 nd stage	$gm(N6) \cdot (rout(N5+N4) (N6))$	rout(N6)	rout(N5)	rout(N4)		gm(N6)				
		9.74E+06	3.22E+03	3.00E+06		9.33E-05	3007079.36	9.74E+06	2297537.69223913	214.34717072
DC gain of 3 rd stage	$gm(P4) \cdot (rout(P3) (P4+N7))$	rout(P4)	rout(N7)	rout(P3)		gm((P4)				
		1.29E+07	7.14E+06	1.57E+07		8.89E-05	19995890	1.57E+07	8807104.40420547	782.67679988
DC gain of 4 th stage	$gm(Np) \cdot (Np)$	rout(Np)				gm(Np)				
		327.111				3.08E-01	327.111			100.7174769

GAIN PLOT AND PHASE PLOT(Without AUX)

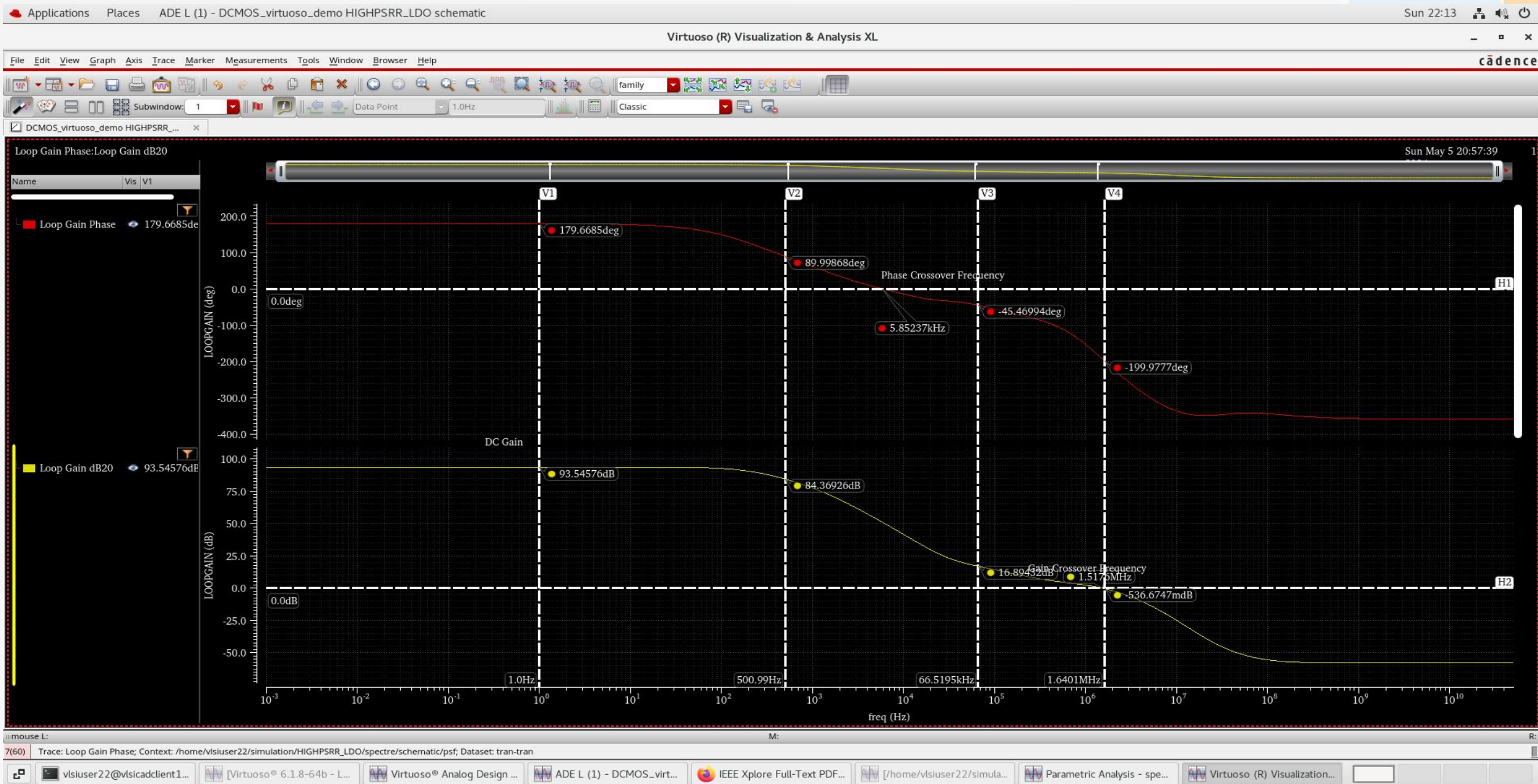

❑ PSRR PLOT(Without AUX)

 

REFERENCE TABLE PAPER

1. <https://ieeexplore.ieee.org/document/8369352/authors#authors>
2. <https://ieeexplore.ieee.org/document/10212011>
3. <https://ieeexplore.ieee.org/document/5419190>
4. <https://ieeexplore.ieee.org/document/9745733>
5. <https://ieeexplore.ieee.org/document/5617585>
6. <https://ieeexplore.ieee.org/document/9036907>

THANK YOU

A decorative graphic on the right side of the slide, consisting of several overlapping, curved, wavy shapes in shades of light blue, yellow, and a darker blue at the bottom right corner.